



BME

Budapest University of Technology and Economics



KJIT

Faculty of Transportation Engineering and Vehicle Engineering

Department of Control for Transportation and Vehicle Systems

Electronics - electronic measuring systems

Transient responses, 3 phase circuits

Ernő Simonyi


simonyi.erno@sztaki.mta.hu

Transient responses(1)

Sudden change in DC voltage when wired in series with a resistor


Capacitor response

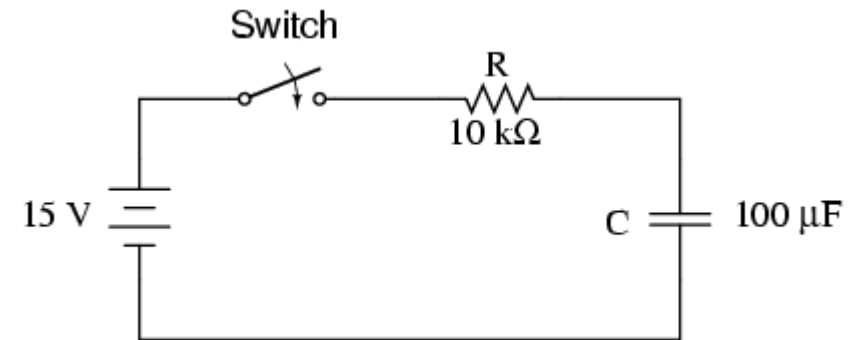- Capacitors store energy in the form of charges (electric field) – small batteries
- Fully discharged – zero volts on terminals
- Fully charged – voltage of the applied voltage source on terminals
- Current acts in reverse compared to voltage



Capacitor response

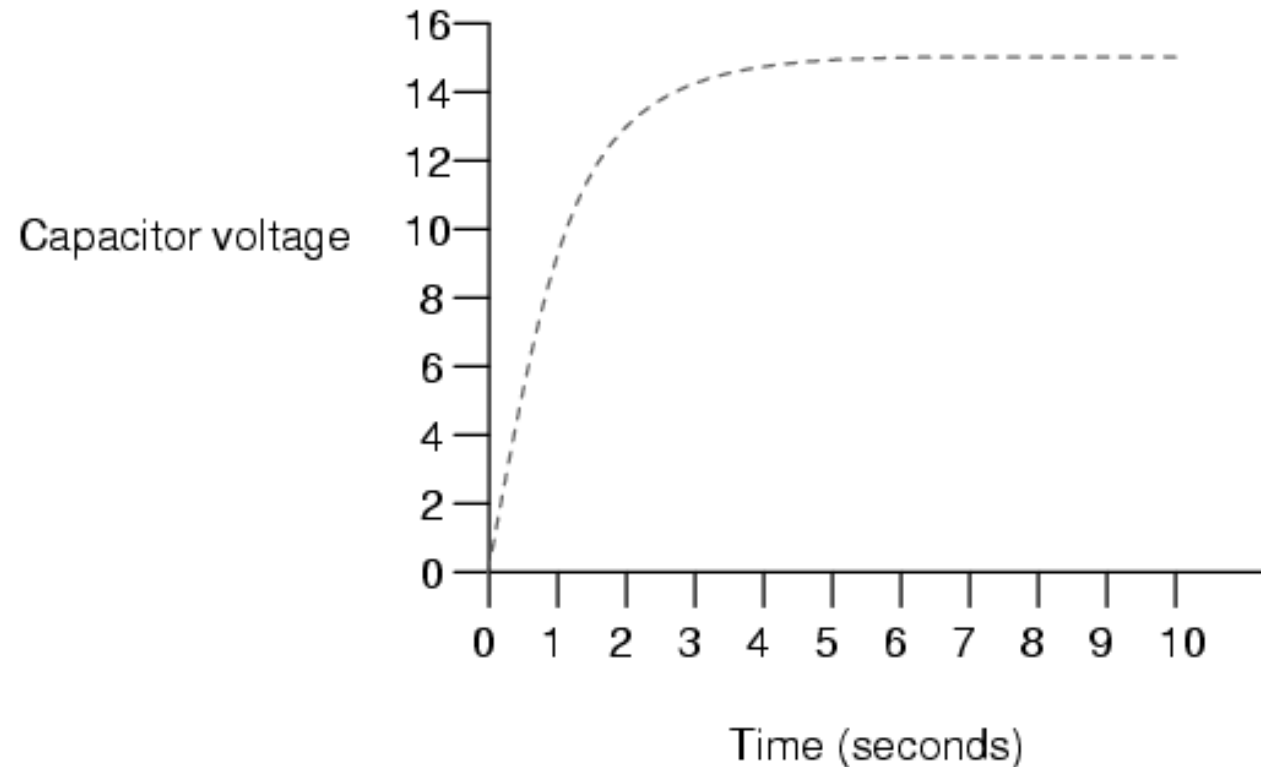- Voltage goes from 0 to maximum
- Current goes from peak to 0



Capacitor response

Time (seconds)	Battery voltage	Capacitor voltage	Current
0	15 V	0 V	1500 μ A
0.5	15 V	5.902 V	909.8 μ A
1	15 V	9.482 V	551.8 μ A
2	15 V	12.970 V	203.0 μ A
3	15 V	14.253 V	74.68 μ A
4	15 V	14.725 V	27.47 μ A
5	15 V	14.899 V	10.11 μ A
6	15 V	14.963 V	3.718 μ A
10	15 V	14.999 V	0.068 μ A


Capacitor response

- Capacitors act somewhat like batteries when faced with a sudden change in applied voltage: they initially react by producing a high current which tapers off over time.
- A fully discharged capacitor initially acts as a short circuit. After charging fully to the supplied voltage, it acts as an open circuit.
- In a resistor-capacitor charging circuit, capacitor voltage goes from nothing to full source voltage, current goes from maximum to zero, both variables changing rapidly at first, approaching their final values slower and slower as time goes on.

Transient responses(2)

Inductor response

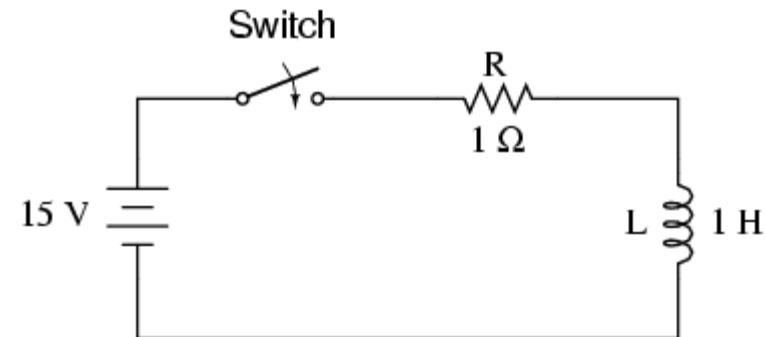- Inductors store energy in the form of a magnetic field – small batteries
- Fully discharged (no magnetic field) – zero current
- Fully charged – current rises to maximum
- Voltage acts in reverse compared to current



Inductor response

- Voltage goes from peak to 0
- Current goes 0 peak to peak



Inductor response

Time (seconds)	Battery voltage	Inductor voltage	Current
0	15 V	15 V	0
0.5	15 V	9.098 V	5.902 A
1	15 V	5.518 V	9.482 A
2	15 V	2.030 V	12.97 A
3	15 V	0.747 V	14.25 A
4	15 V	0.275 V	14.73 A
5	15 V	0.101 V	14.90 A
6	15 V	37.181 mV	14.96 A
10	15 V	0.681 mV	14.99 A

Inductor response

- A fully discharged inductor (no current through it) initially acts as an open circuit with the sudden application of voltage. After charging fully, it acts as a short circuit.
- In a resistor-inductor “charging” circuit, inductor current goes from nothing to full value while voltage goes from maximum to zero, both variables changing rapidly at first, approaching their final values slower and slower as time goes on.

Transient responses(3)

- *time constant* of the circuit: the amount of time it takes for voltage or current values to change approximately 63 percent from their starting values to their final values in a transient situation.

For resistor-capacitor circuits:

$$\tau = RC$$

For resistor-inductor circuits:


$$\tau = \frac{L}{R}$$

Transient responses(3)

- Charging functions: $V(t) = V_0(1 - e^{-t/\tau})$
- Discharging functions: $V(t) = V_0(e^{-t/\tau})$
 - V_0 - peak voltage
 - Same for current


Three-phase circuits

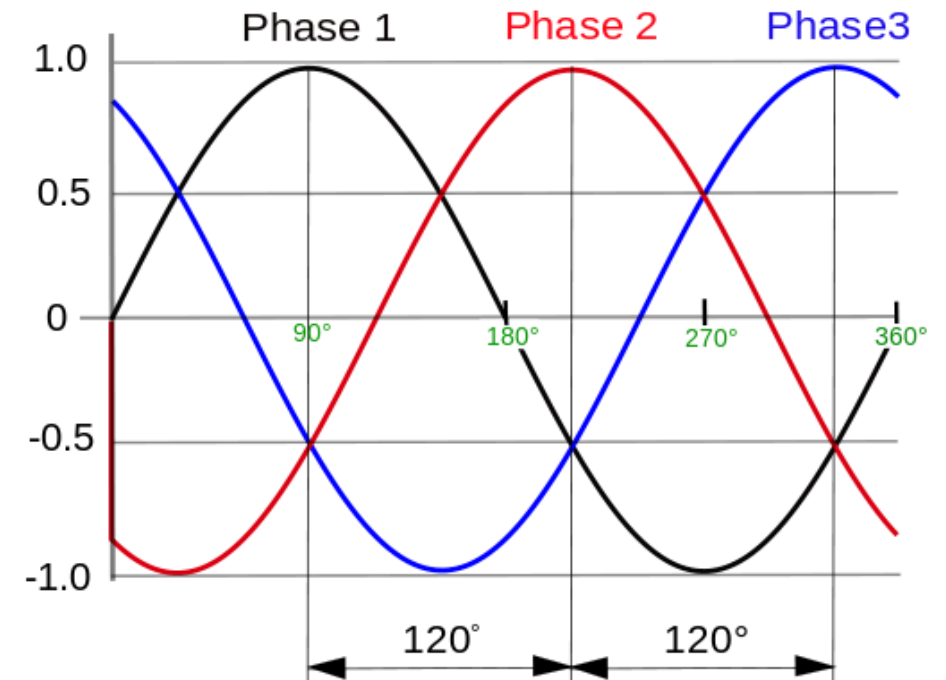- **3 separate AC phases with same volume a 120° phase difference**
 - Assymmetric systems lack the advantages of a symmetric one
- Common reference connected to ground
- Load can be symmetric or asymmetric
- Phase currents can cancel out each other
- Power transfer on linear loads is constant
- Can produce a rotating magnetic field



Three-phase circuits

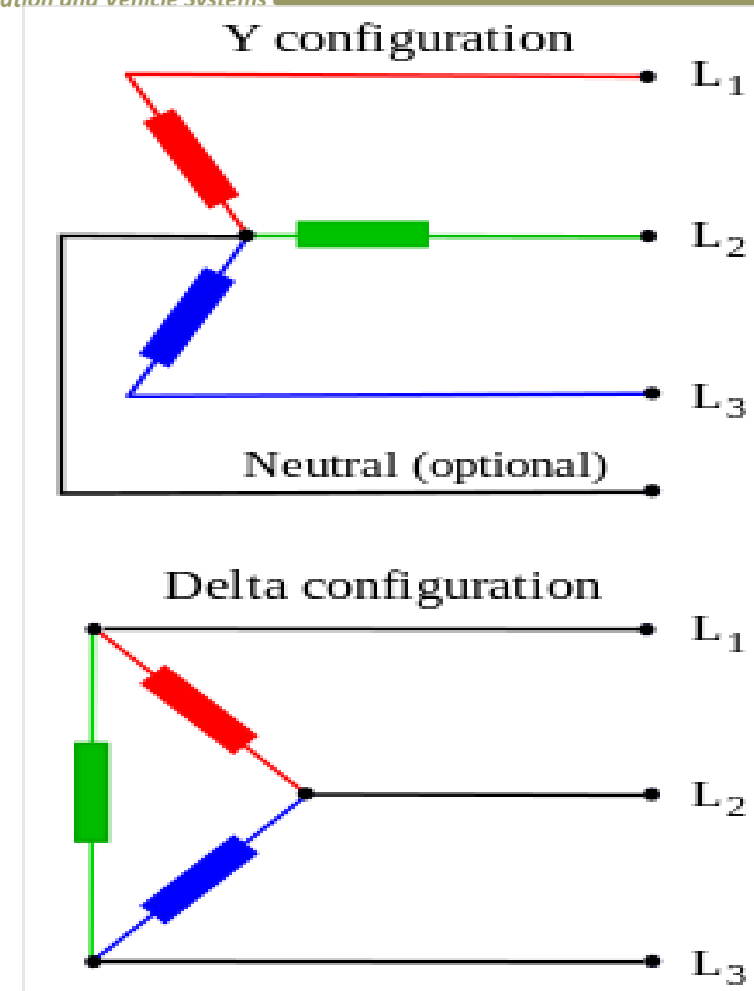- 2 separate configurations
 - Line and phase voltages/currents
- Phase – between a phase and neutral
- Line – between 2 lines
- Y configuration
 - $U_{LL} = \sqrt{3}U_{LN}$
 - $I_{LL} = I_{LN}$
- Delta configuration
 - $I_{LL} = \sqrt{3}I_{LN}$
 - $U_{LL} = U_{LN}$



Three-phase circuits

- Both configurations
 - $P = 3U_{LN}I_{LN} \cos \varphi$
 - $P = \sqrt{3}U_{LL}I_{LL} \cos \varphi$