



**BME**



**KJT**

*Budapest University of Technology and Economics*

*Faculty of Transportation Engineering and Vehicle Engineering*

*Department of Control for Transportation and Vehicle Systems*

# Electronics - electronic measuring systems

Four poles, diodes and transistors

Ernő Simonyi

[simonyi.erno@sztaki.mta.hu](mailto:simonyi.erno@sztaki.mta.hu)


# Four poles

**Two poles:**

Circuits with two terminals (1 pair)

**Four poles:**

Circuits with 4 terminals (2 pairs)

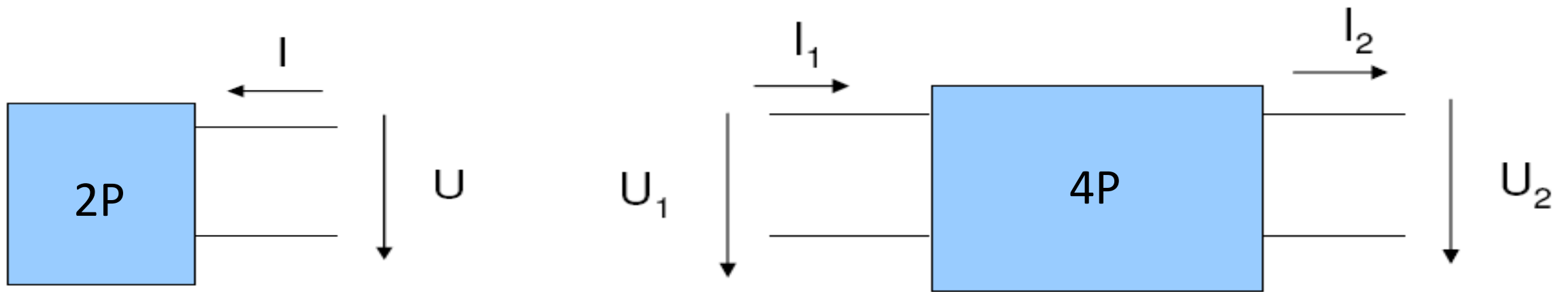

# Four poles

## 2 pole characteristics

Impedance ( $Z$ ); Admittance ( $Y$ )

$$V = ZI; \quad I = YV$$

$$Z = \frac{V}{I}; \quad Y = \frac{I}{V}$$

# Four poles

## 4 pole characteristics

Parametric equations ( $V \sim U$ )

Impedance ( $Z$ ); Admittance ( $Y$ ), Chain ( $A$ ), Hybrid ( $H$ )

**Impedance parameters:**

$$U_1 = Z_{11} I_1 + Z_{12} I_2$$

$$U_2 = Z_{21} I_1 + Z_{22} I_2$$

# Impedance parameters

## Impedance parameters

$$Z_{11} = \frac{U_1}{I_1} \text{ if } I_2 = 0$$

$$Z_{12} = \frac{U_1}{I_2} \text{ if } I_1 = 0$$

$$Z_{21} = \frac{U_2}{I_1} \text{ if } I_2 = 0$$

$$Z_{22} = \frac{U_2}{I_2} \text{ if } I_1 = 0$$

# Admittance parameters

## Admittance parameters

$$I_1 = Y_{11}U_1 + Y_{12}U_2$$

$$I_2 = Y_{21}U_1 + Y_{22}U_2$$

# Chain parameters

## Chain parameters

$$U_1 = A_{11}U_2 + A_{12}I_2$$

$$I_1 = A_{21}U_2 + A_{22}I_2$$

# Hybrid parameters

## Hybrid parameters

$$U_1 = H_{11} I_1 + H_{12} U_2$$

$$I_2 = H_{21} I_1 + H_{22} U_2$$



# Four poles

## Calculations:

$$U_x = 0 \text{ -- } \textit{short circuit}$$

$$I_x = 0 \text{ -- } \textit{open circuit}$$


# Diodes

- **Diode** is a very basic but important semiconductor device
  - Two different layers
  - Mostly made from Silicon or Germanium
- Semiconductors – materials that can either allow or stop the flow of current

# Semiconductor Basics

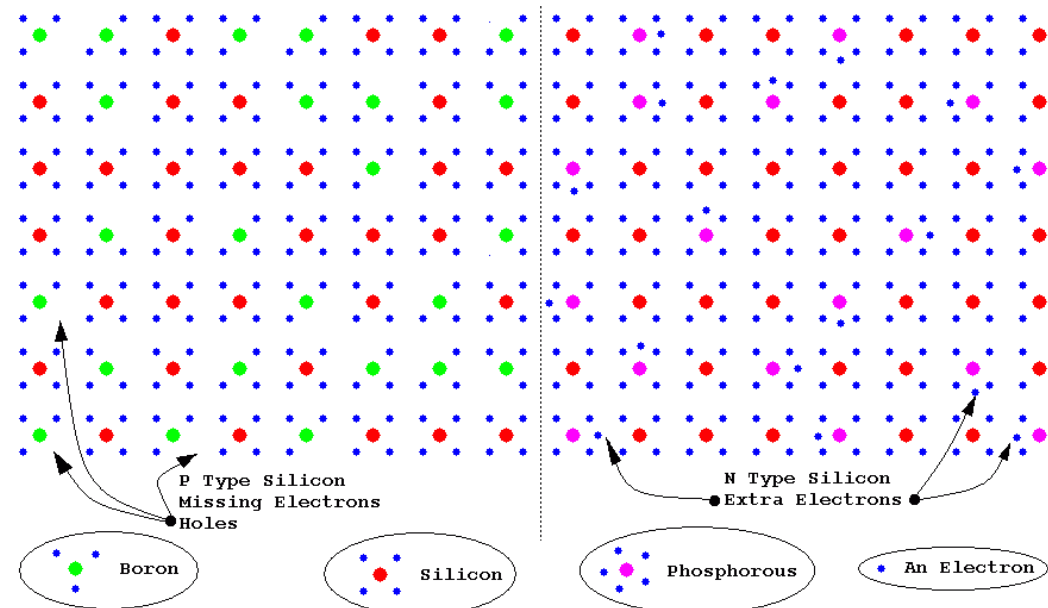
## Two types of intrinsic carriers

- Electrons (n) and holes (p)
- In an intrinsic (no doping) material,  $n=p$
- Use doping to improve conductivity



# Diodes


## Simplified structure

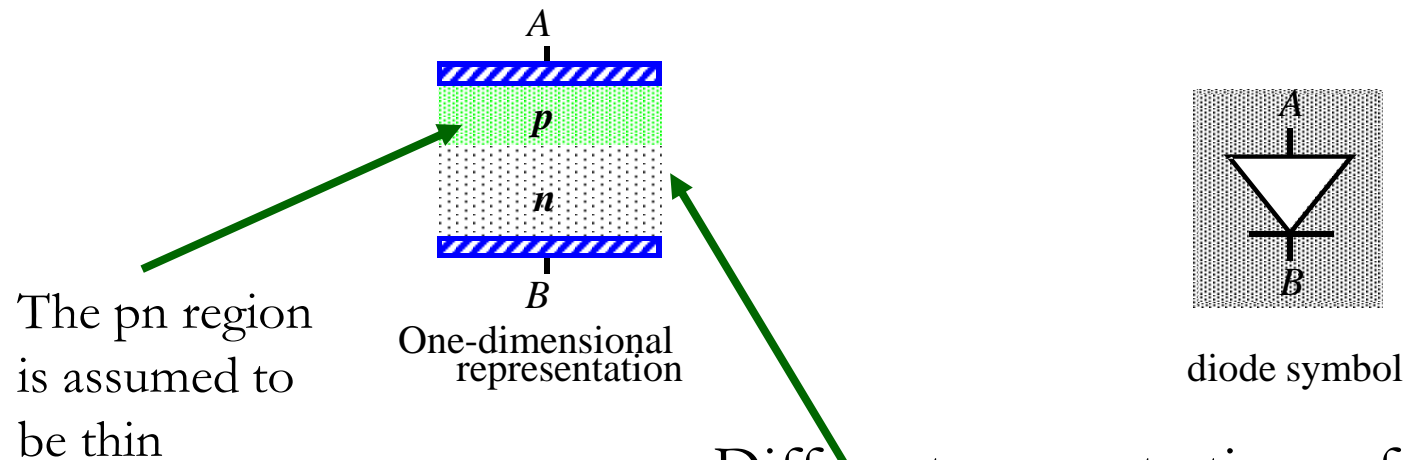

Different concentrations of electrons (and holes) of the p and n-type regions cause a **concentration gradient** at the boundary
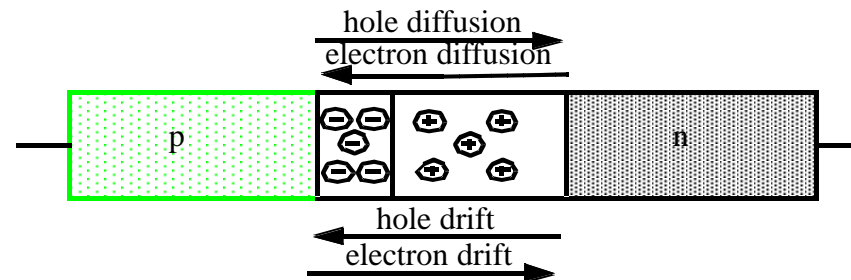
# Diodes

- Concentration Gradient causes electrons to diffuse from n to p, and holes to diffuse from p to n
- This produces immobile ions in the vicinity of the boundary
- Region at the junction with the charged ions is called the **depletion region or space-charge region**



# Diodes

- Forward Bias:**
- $V_{\text{applied}} > 0$**
- In forward bias the depletion region shrinks slightly in width.
  - With this shrinking the energy required for charge carriers to cross the depletion region decreases exponentially.
  - Therefore, as the applied voltage increases, current starts to flow across the junction.



# Diodes

**Reverse bias**

**$V_{\text{applied}} < 0$**

- Under reverse bias the depletion region widens.
- A small leakage current,  $I_s$  (saturation current) flows under reverse bias conditions. This saturation current is made up of electron-hole pairs being produced in the depletion region.




# Diodes

Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering

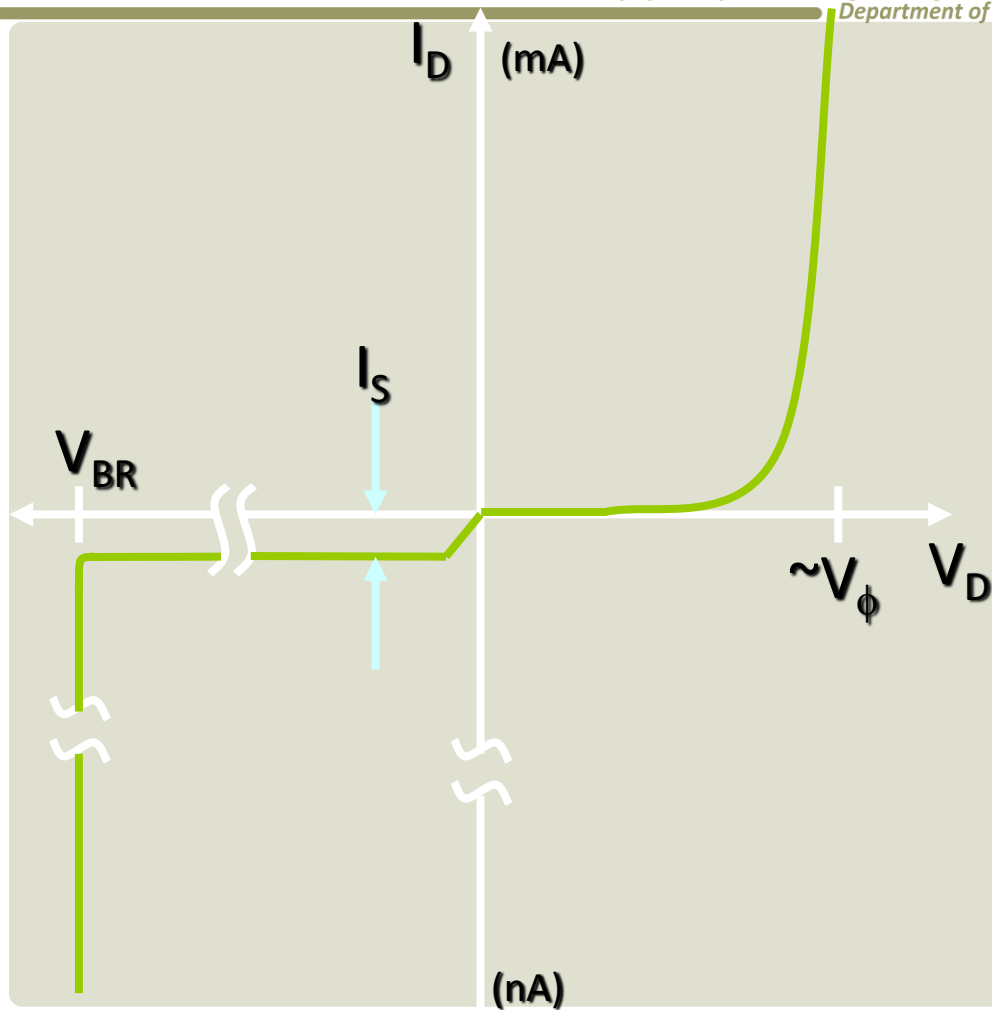Department of Control for Transportation and Vehicle Systems



- $V_D$  = Bias Voltage
- $I_D$  = Current through Diode.  $I_D$  is Negative for Reverse Bias and Positive for Forward Bias
- $I_S$  = Saturation Current
- $V_{BR}$  = Breakdown Voltage
- $V_\phi$  = Barrier Potential Voltage




# Diodes

Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering

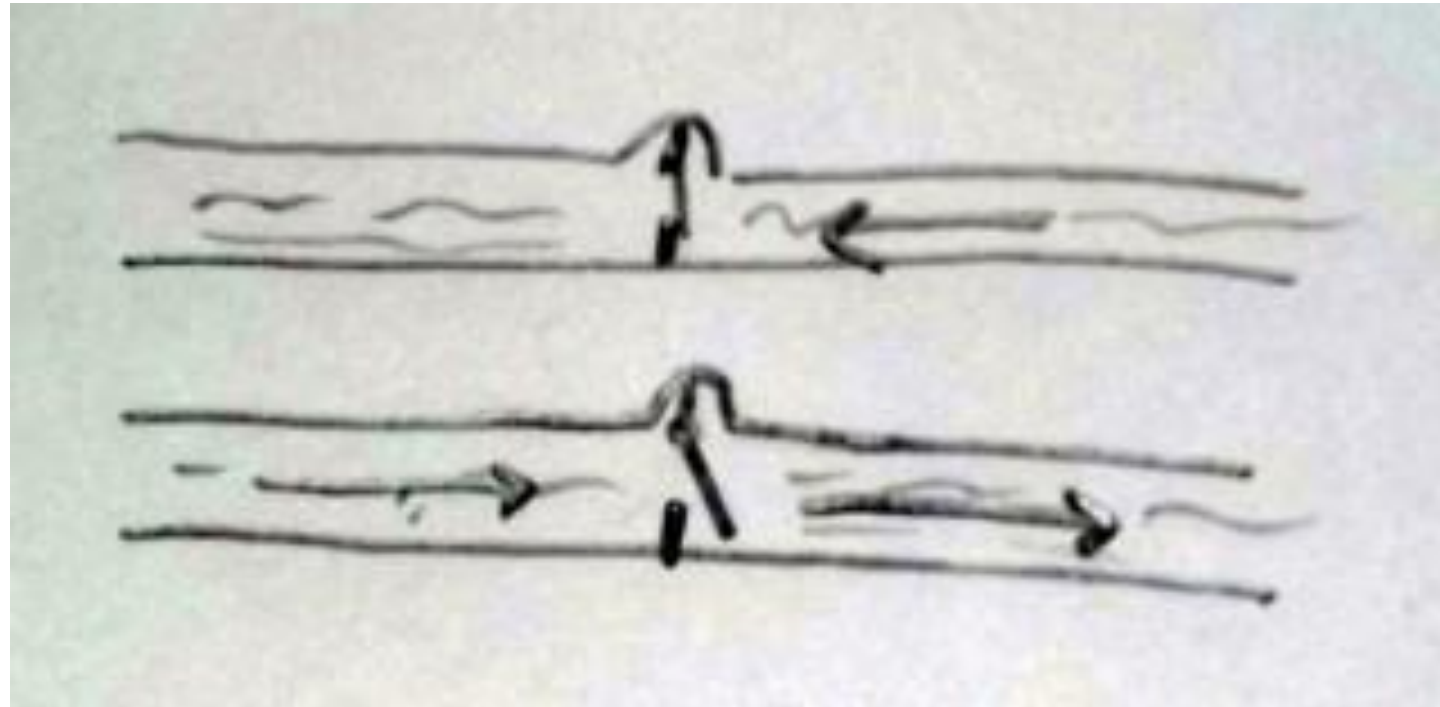Department of Control for Transportation and Vehicle Systems



# Zener diodes

## Zener diodes

- Works as a regular diode in the forward bias
- But are intended to operate in the breakdown region
- Used as a voltage stabilizer




# Transistors

## Transistors

- 3 layered semi-conductors
- FET – Field Effect Transistors
  - Can occupy less chip area, is more easily fabricated
- BJT – Bipolar Junction Transistors
  - Can produce large output currents
- Both are used in amplifiers and logic gates
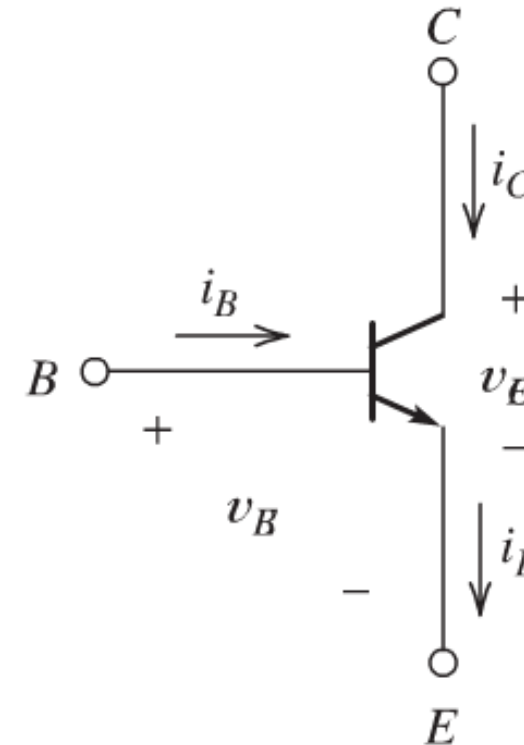
# BJT

- Can be npn or pnp
- 3 legs/layers
  - Base
  - Emitter
  - Collector
- Multiple build variations
- 2 mode of use
  - Switch or linear/amplifier modes



# Transistors

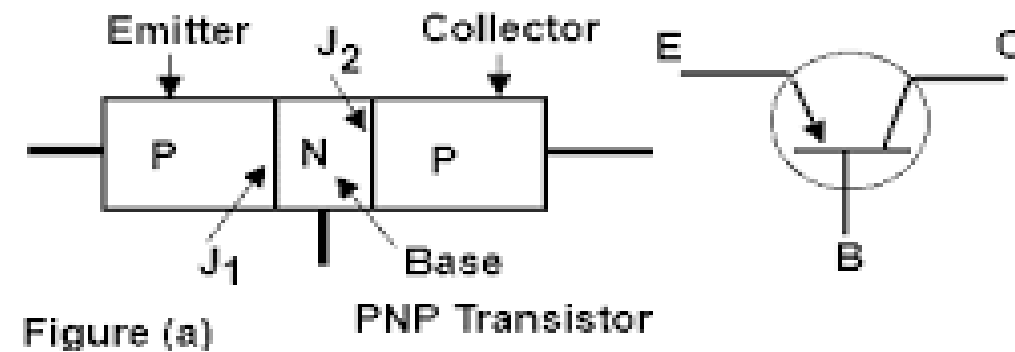
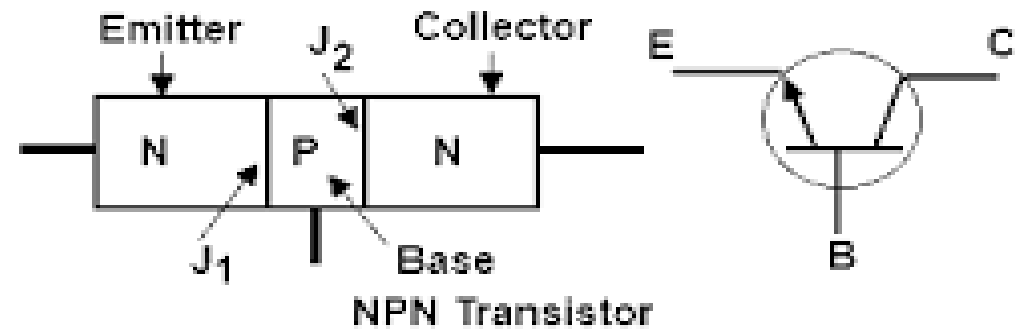


Figure (a)

# Transistors

## How does it work?


A combination of a PN and an NP layer

- When the transistor conducts, electrons are attracted from the emitter by holes appearing in the base. A few electrons will combine with holes to form base current, which is indicated by a few free electrons flowing around the base–emitter circuit.
- With  $V_{ce}$  turned on, the majority of free electrons in the base area are attracted across the collector–base depletion layer to form the large current flowing in the collector–emitter circuit.
- As a small base current, caused by forward biasing the base–emitter junction causes a large collector current to flow, the transistor is acting as a current amplifier.

$$i_c = \beta i_B$$

[http://www.learnabout-electronics.org/Semiconductors/bjt\\_04.php](http://www.learnabout-electronics.org/Semiconductors/bjt_04.php)

# Transistor characteristics

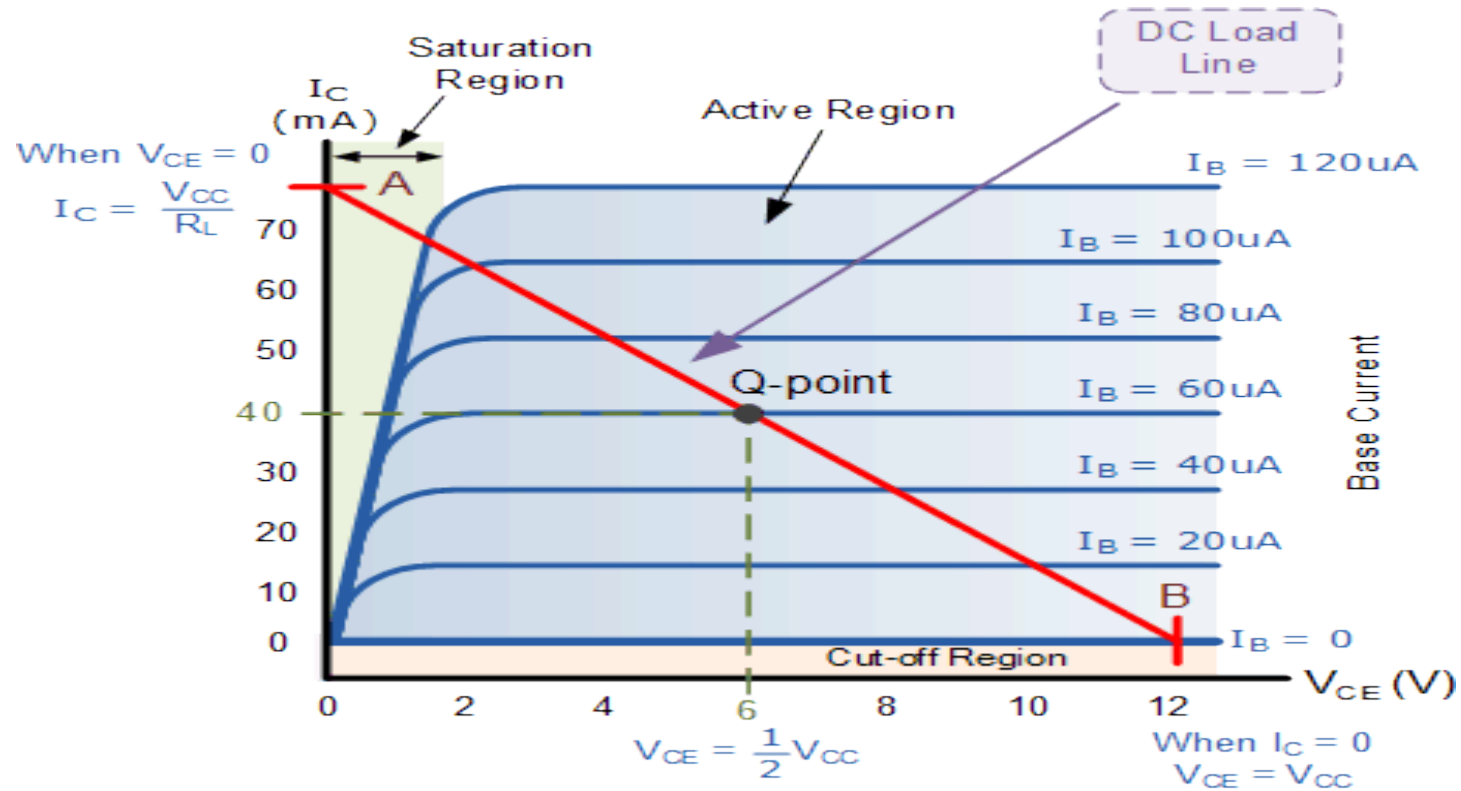

# Amplifiers

## Amplify input voltage or current

Operational amplifier

