

IC TECHNOLOGY


Lecture 2.

Budapest University of Technology and Economics Faculty of Transportation Engineering and Vehicle Engineering

Department of Control for Transportation and Vehicle Systems

- Integrated Circuit: An integrated circuit (IC, a chip, or a microchip) is a set of electronic circuits on one small flat piece (or "chip") of semiconductor material, normally silicon.
- First IC had created by Jack Kilby researcher of Texas Instruments

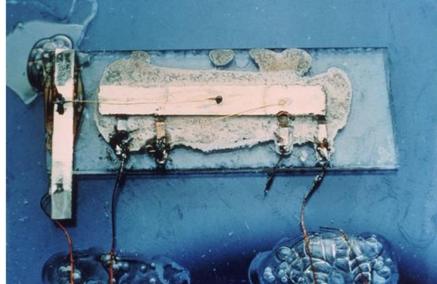 in 1958.
- Basic elements of ICs:
 - resistor,
 - capacitor,
 - diode,
 - transistor.




Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering Department of Control for Transportation and Vehicle Systems

• First silicon IC: Robert Noyce, 1961




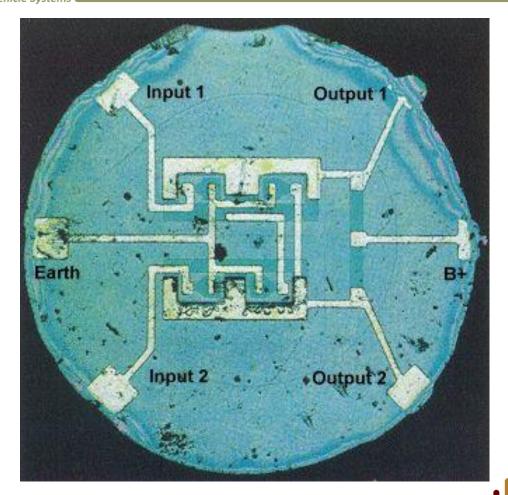

Budapest University of Technology and Economics Faculty of Transportation Engineering and Vehicle Engineering

Department of Control for Transportation and Vehicle Systems

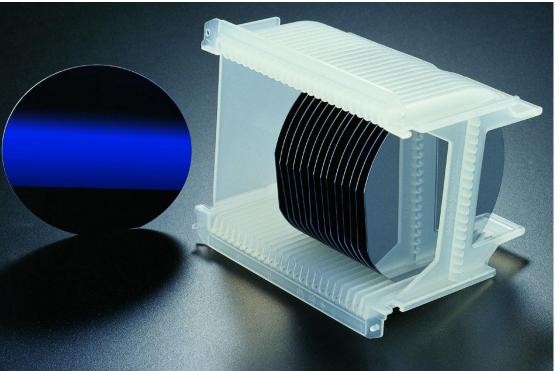- Digital integrated circuits can contain anywhere from one to billions of logic gates, flip-flops, multiplexers, and other circuits in a few square millimeters.
- Planar process (several times in a row), from slices of a silicon single crystal rod, called wafer:
 - creation of a layer,
 - lithography,
 - doping.




Budapest University of Technology and Economics Faculty of Transportation Engineering and Vehicle Engineering Department of Control for Transportation and Vehicle Systems

- Planar means, that the production of ICs take place in planar layout.
- Creation of a layer: chemical or physical methods in order to create a contigous layer on the wafer:
 - oxidation, epitaxial growth, chemical vapor deposition, physical vapor deposition,
 - SiO₂ layer: masks and insulates

Budapest University of Technology and Economics Faculty of Transportation Engineering and Vehicle Engineering

Department of Control for Transportation and Vehicle Systems

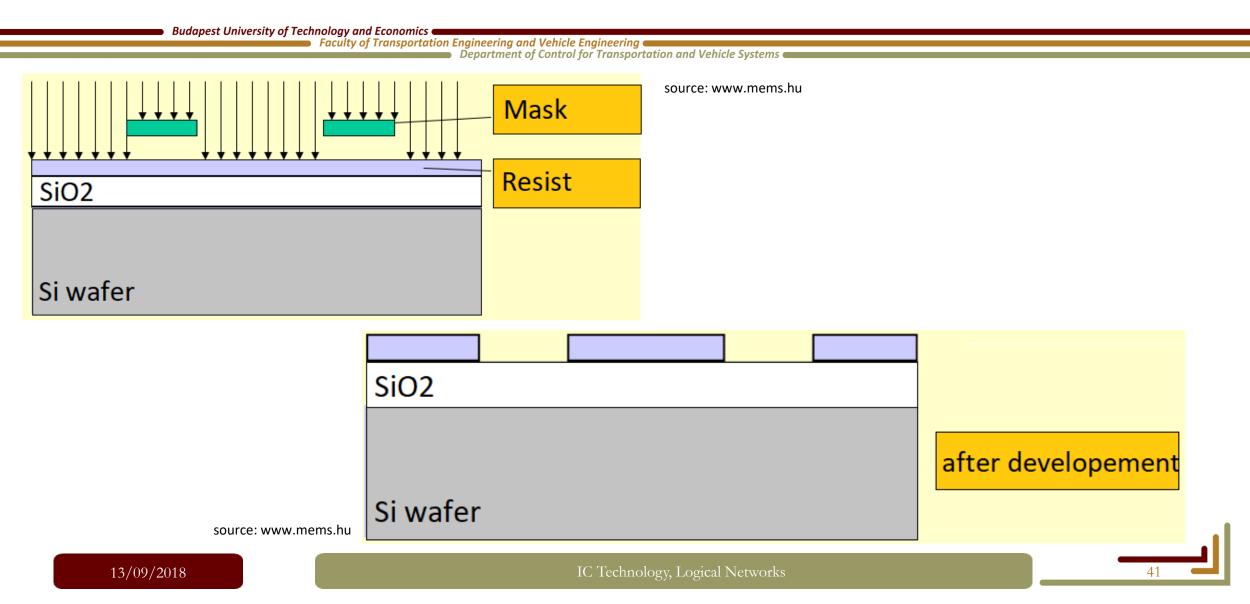
- Litography process: the purpose is to create the pattern,
- Steps of the litography process:
 - applying fotoresist material to the wafer,
 - pattern mapping,:
 - the wafer is illuminated through a mask belonging to the given layer,
 - where light penetrates the material, it will polymerize, so it will be resistant to some solvents.
 - oxide milling.



Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering

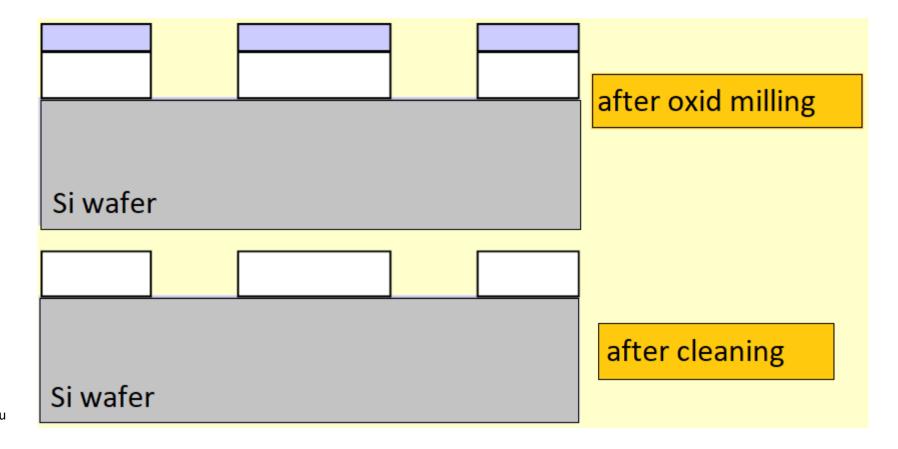Department of Control for Transportation and Vehicle Systems




source: www.mems.hu

13/09/2018


Budapest University of Technology and Economics
Faculty of Transportation Engineering and Vehicle Engineering

Department of Control for Transportation and Vehicle Systems

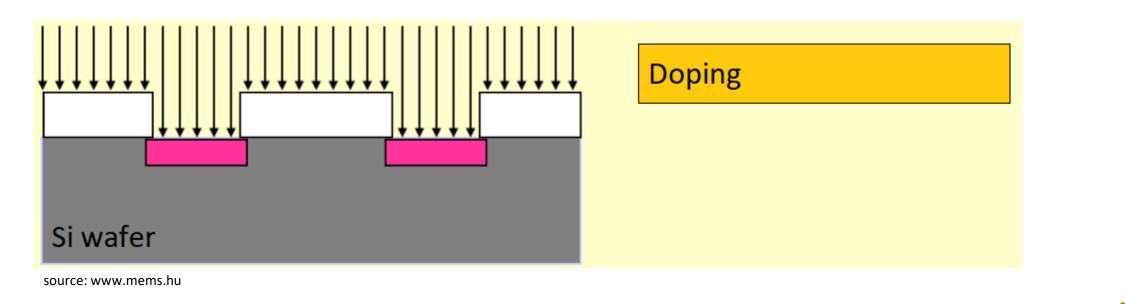- Doping: with n or p type materials:
 - diffusion and ion implantation





13/09/2018

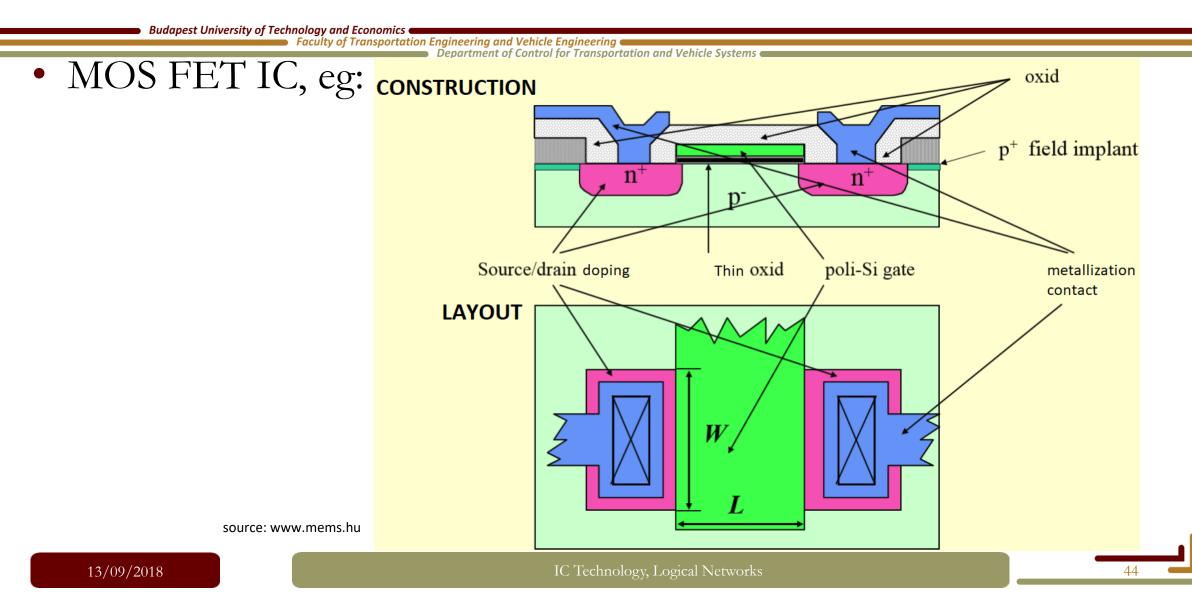

Budapest University of Technology and Economics

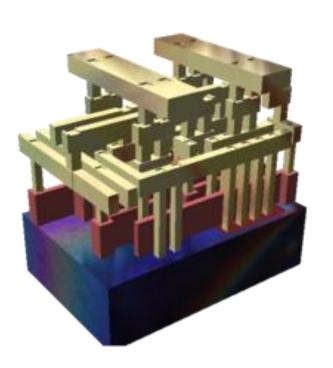Faculty of Transportation Engineering and Vehicle Engineering
 Department of Control for Transportation and Vehicle Systems




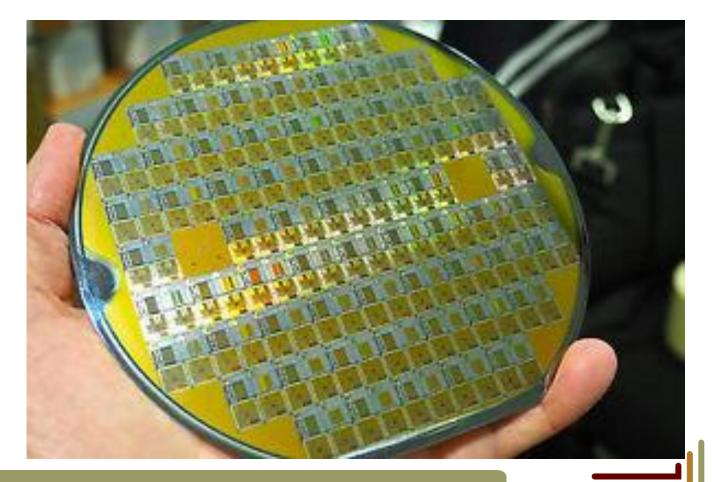

Budapest University of Technology and Economics Faculty of Transportation Engineering and Vehicle Engineering

Department of Control for Transportation and Vehicle Systems

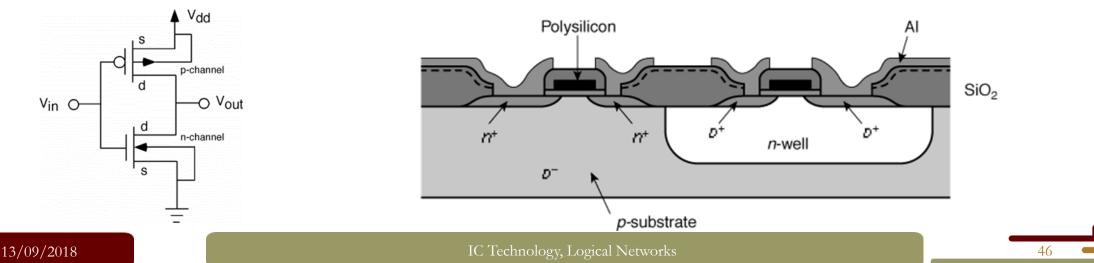
- CMOS type inverter:
 - p and n type layers by masks these are the layers of the source and the drain of the transistors, with aluminum outlet,
 - gate of the transistor is made by polycrystalline silicon, beneath a thin layer of SiO_2 , above it is also a thicker insulating layer.



Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering

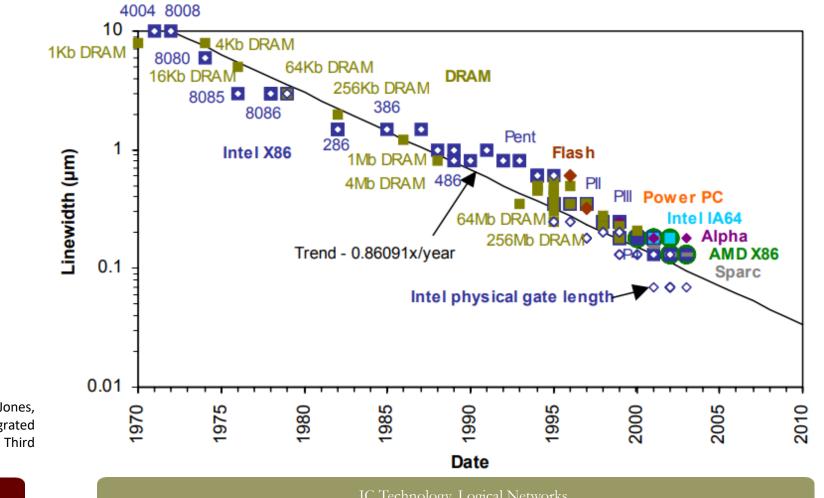Department of Control for Transportation and Vehicle Systems



source: Scotten W. Jones, Introduction to Integrated CircuitTechnology, Third Edition, 2004


13/09/2018


Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering Department of Control for Transportation and Vehicle Systems

• IC enclosures:

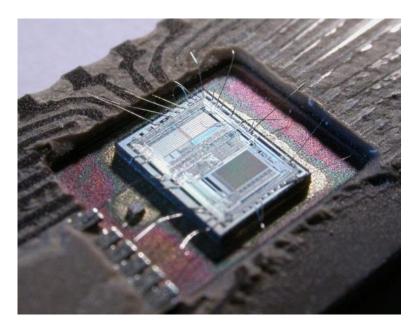- according to assembling technology:
 - through-hole,
 - surface-mounted:
 - dual,
 - quad,
 - ball grid array,
 - contactless,
- according to the material used:
 - plastic,
 - ceramic,
 - metal and power.



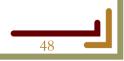

C Technology, Logical Networks

13/09/2018

Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering



SOP (Small Outline Package)



DIP (Dual In Line)



PLCC (Plastic Leaded Chip Carrier)




SSOP (Small Schrink Outline Package)

Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering

- Generation of ICs:
- ICs number of transistors:
 - SSI (Small-Scale Integration): 10x
 - MSI (Medium-Scale Integration): 100x
 - LSI (Large-Scale Integration): 10000x
 - VLSI (Very Large-Scale Integration): 100000x
 - ULSI (Ultra Large-Scale Integration): 1000000x
 - SoC (System on Chip): a "whole computer" integrated in a single IC. (E.g.: motherboard of smart phones)
 - Intel 4004 (1971): 2300
 - Intel Core i7 (2008): 781 million
 - Intel Core i9 (2017): about 7 billion
- Line width in the chip:
 - Intel 4004 (1971): 10 μm
 - Intel Core i7 (2008): 45 nm
 - Intel Core i9 (2017): 10 nm

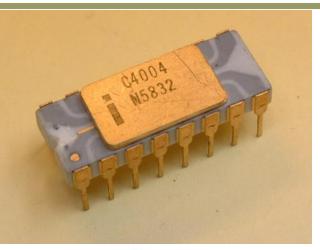



13/09/2018

Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering

Department of Control for Transportation and Vehicle Systems

- Memories:
- Volatile:
 - RAM (Random Access Memory):
 - Dynamic RAM,
 - Static RAM.
- Non Volatile:
 - ROM (Read-Only Memory),
 - PROM (Programmable ROM),
 - EPROM (Erasable Programmable ROM),
 - EEPROM (Electrically Erasable Programmable ROM),
 - Flash.

Budapest University of Technology and Economics Faculty of Transportation Engineering and Vehicle Engineering


Department of Control for Transportation and Vehicle Systems


- RAM:
 - Dynamic RAM:
 - one cell consists of one transistor and one capacitor,
 - it has to refresh time to time, because the capacitor is discharged due to the trickle current,
 - slow, smaller size, cheap.
 - Static RAM:
 - one cell consists of more transistors (flip-flop),
 - it stores the data for any length of time, if there is a power supply,
 - fast, small energy consumption, expensive.

Budapest University of Technology and Economics
Faculty of Transportation Engineering and Vehicle Engineering

Department of Control for Transportation and Vehicle Systems

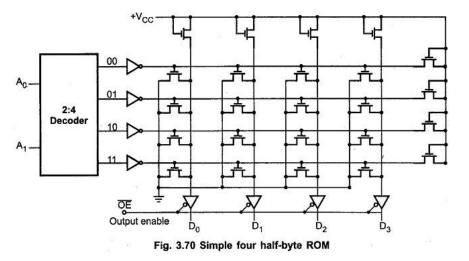- ROM
 - Programmed by the manufacturer, the user can only read it.
- PROM
 - User can program it once, than he can only read it.




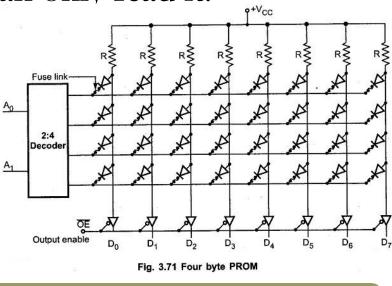


Budapest University of Technology and Economics Faculty of Transportation Engineering and Vehicle Engineering

Department of Control for Transportation and Vehicle Systems

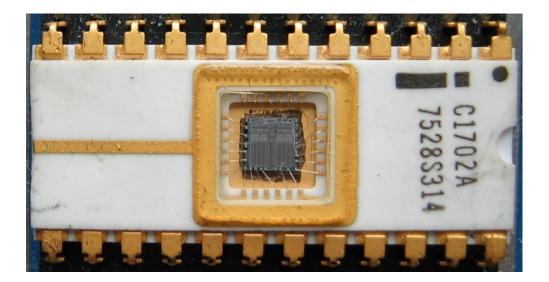- EPROM
 - Cleared by UV light, programmed by special equipment.
- EEPROM
 - Programmed and cleared by special equipment.
- Flash
 - Type of EEPROM, programmed and cleared by the computer.



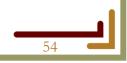source: By Author : Poil 01:10, 17 Apr 2005 (UTC) - Author personnal collection., CC BY-SA 3.0, https://commons.wikimedia.org/w/index.php?curid=97658



13/09/2018



LOGICAL NETWORKS

Lecture 2.

Boolean Algebra

Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering

Department of Control for Transportation and Vehicle Systems

• Logical connectives:

$$0 \cdot 0 = 0 \cdot 1 = 1 \cdot 0 = 0; \qquad 1 \cdot 1 = 1$$

$$0 + 1 = 1 + 0 = 1 + 1 = 1; \qquad 0 + 0 = 1$$

$$\bar{0} = 1; \quad \bar{1} = 0; \quad \bar{0} = 0; \quad \bar{1} = 1$$



Boolean Algebra

Budapest University of Technology and Economics	
Faculty of Transportation Engineering and Vehicle Engineering Department of Control for Transportation and Vehicle Systems	
• commutativity:	
A + B = B + A	
$A \cdot B = B \cdot A$	
• associavity:	
A + B + C = A + (B + C)	
$A \cdot B \cdot C = A \cdot (B \cdot C)$	
• absorption:	
$A + A \cdot B + A \cdot B \cdot C + \dots = A$	
$A \cdot A + B \cdot A + B + C \cdot \dots = A$	
• distibutivity:	
$A \cdot (B + C) = A \cdot B + A \cdot C$	
$A + (B \cdot C) = (A + B) \cdot (A + C)$	
$A \cdot A + A \cdot C + B \cdot A + B \cdot C = A \cdot (1 + C + B) + BC$	
• De Morgan's laws:	
$\overline{A + B} = \overline{A} \cdot \overline{B}$	
$\overline{A \cdot B} = \overline{A} + \overline{B}$	
	- II.

IC Technology, Logical Networks


57


Realization of Logical Networks

Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering

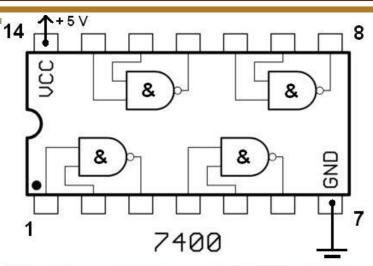
- logical gates:
 - basic functions
 - AND, OR, NOT
 - complex functions
 - NAND, NOR, XOR (exclusive OR), XNOR (exclusive NOR)
- relay
- computers
- pneumatic networks



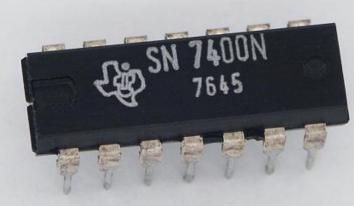



Realization of Logical Networks

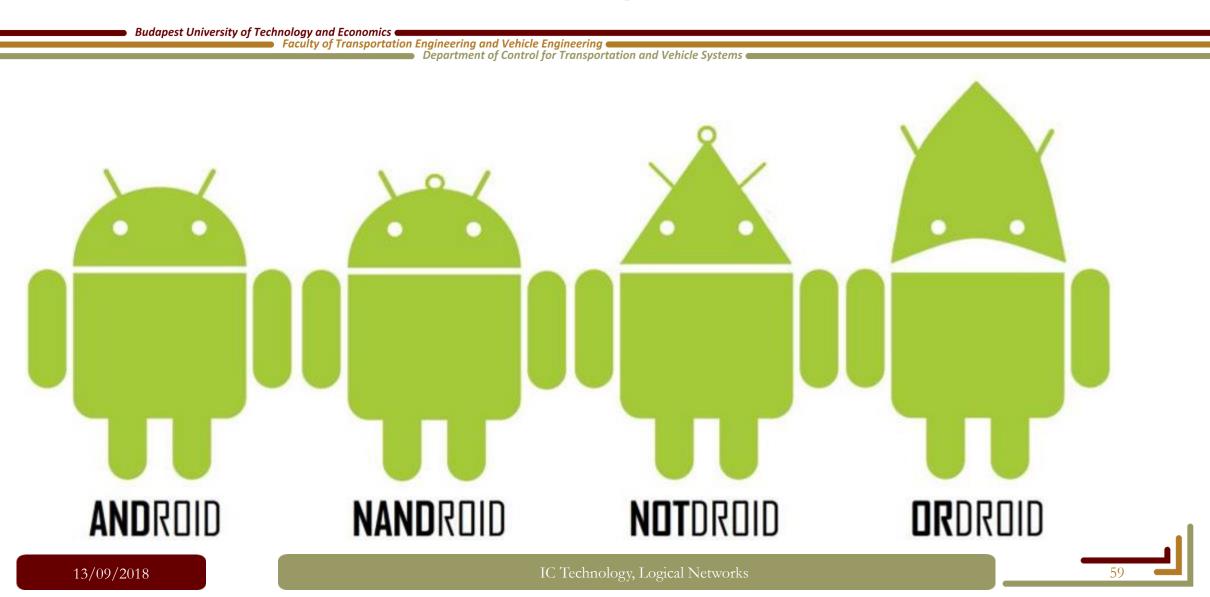


Realization of Logical Networks

Budapest University of Tech	nology and Economics Faculty of Transportation Engineering and Vehicle Engineering Department of Control for Transportatio			
	NOT	on and Vehicle Systems	-1-	
	AND		& -	
	OR		1	
	NAND		_& ⊳	
	NOR		1 ⊸	
	XOR		_ __	
	XNOR			
12/00/2019	IC Technolog	y Logical Notworks		

Budapest University of Technology and Economics Faculty of Transportation Engineering and Vehicle Engineering Department of Control for Transportation and Vehicle Systems

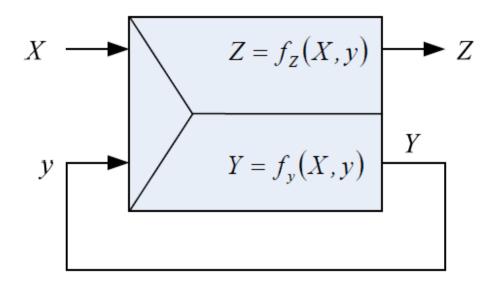• sequential networks: a network, whose output depends on the actual inputs and past inputs (the order of the inputs) – a network with memory






13/09/2018

Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering Department of Control for Transportation and Vehicle Systems

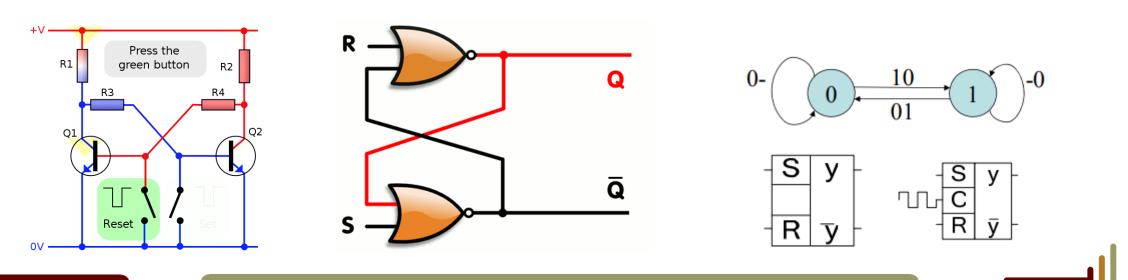- realization with flip-flops (finite state machine):
 - flip flop: a circuit, that has two stable states to store a one bit information, it is a bistable multivibrator, can be synchronous (clock controlled) or asynchronous (event driven),
- SR flip-flop:



Budapest University of Technology and Economics Faculty of Transportation Engineering and Vehicle Engineering

У

 ∇

G

Department of Control for Transportation and Vehicle Systems

• JK flip-flop:

00

)10

11

0-

OR

-0

11


01

OR

-0

0)


• T flip-flop:

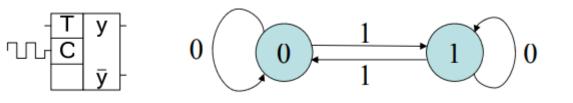

11

01

• D flip-flop:

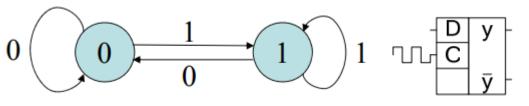


00

01

10

• DG flip-flop:


0

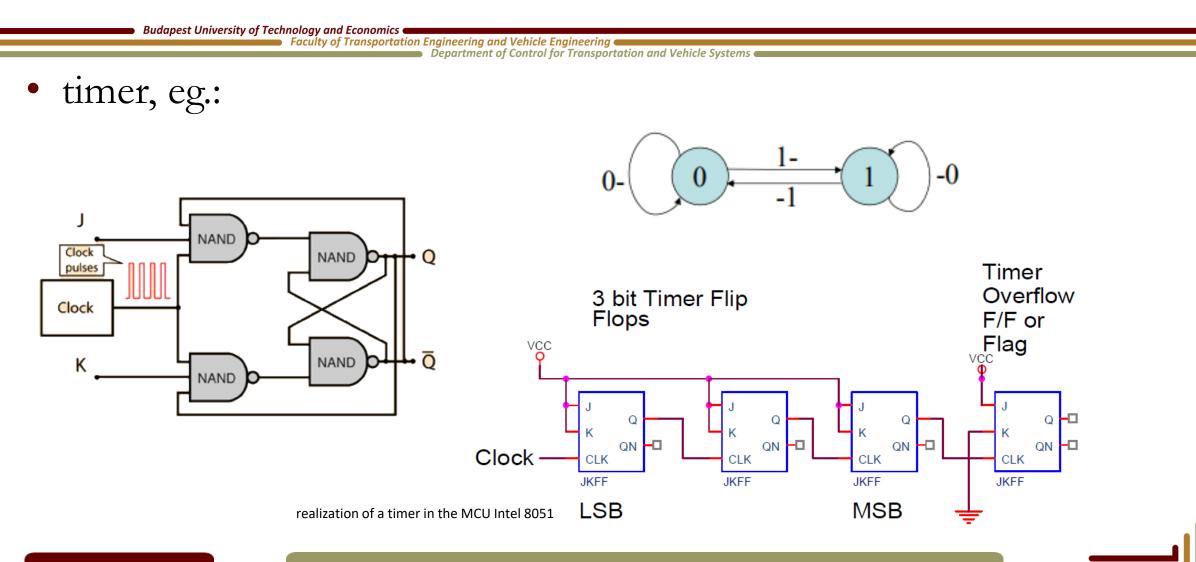

Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering Department of Control for Transportation and Vehicle Systems

• shift register, eg.:

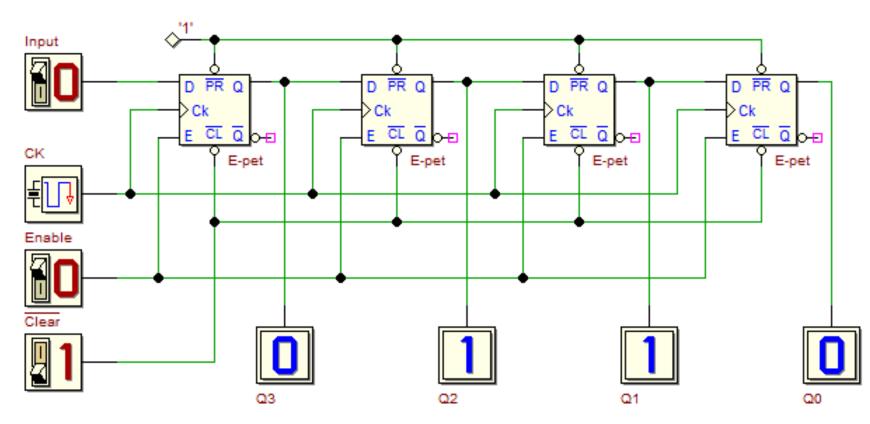


source: https://www.digitalelectronicsdeeds.com/demos/demopage_seq.html



Budapest University of Technology and Economics

Faculty of Transportation Engineering and Vehicle Engineering
 Department of Control for Transportation and Vehicle Systems

binary up counter, eg.: •

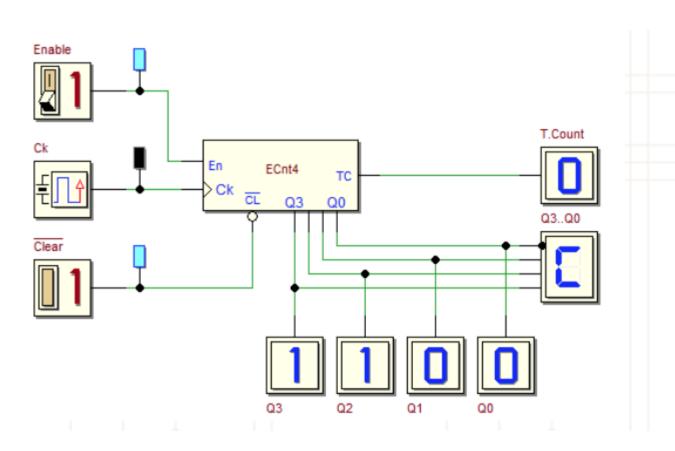

source: https://www.digitalelectronicsdeeds.com/demos/demopage_seq.html

Budapest University of Technology and Economics Faculty of Transportation Engineering and Vehicle Engineering

Department of Control for Transportation and Vehicle Systems

- more examples:
- <u>https://www.allaboutcircuits.com/textbook/digital/chpt-</u> <u>11/finite-state-machines/</u>
- <u>https://www.youtube.com/watch?v=dV8PTOZ2-gQ</u>
- <u>https://www.youtube.com/watch?v=kNlGHmsfp40</u>
- <u>https://www.youtube.com/watch?v=YW-_GkUguMM</u>
- <u>https://www.youtube.com/watch?v=F1OC5e7Tn_o</u>





End of Lecture 2.

Thank you for your attention!